

EE1025-Independent Project

Thevenin's theorem, Norton's theorem Superposition

P.Srijith
EE19BTECH11041
Eshwari.J
EE19BTECH11042

March 4, 2020

Abstract

Simplification is necessary! Solving large and complicated circuits involve theoretical approach using theorem's **Thevenin, Norton, Superposition**. Before directly applying the mathematical equations to the circuits one must know the limitations of these theorems. Each of these theorems have specific conditions and applicable in different situations!

Contents

1	Aim	2
2	Introduction	2
3	Apparatus	3
4	Theoretical Background	4
4.1	Thevenin Theorem	4
4.2	Norton Theorem	4
4.3	Superposition Theorem	4
5	Procedures	5
5.1	Thevenin Theorem	5
5.2	Norton Theorem	5
5.3	Superposition Theorem	6
5.4	Task -1	6
5.5	Task -2	7
5.6	Task 3	8


6	Analysis	11
6.1	Task-1	11
6.2	Task-2	11
6.3	Task-3	11
7	Conclusions	12

1 Aim

- In this experiment, Thevenin, Norton, Superposition theorem are explained.
- Understand the importance of each theorem and how to simplify complicated circuits.
- Know the conditions of Applicability.
- Solve equations theoretically, and compare with experimental results.
- Then verify the experimental and theoretical values.


2 Introduction

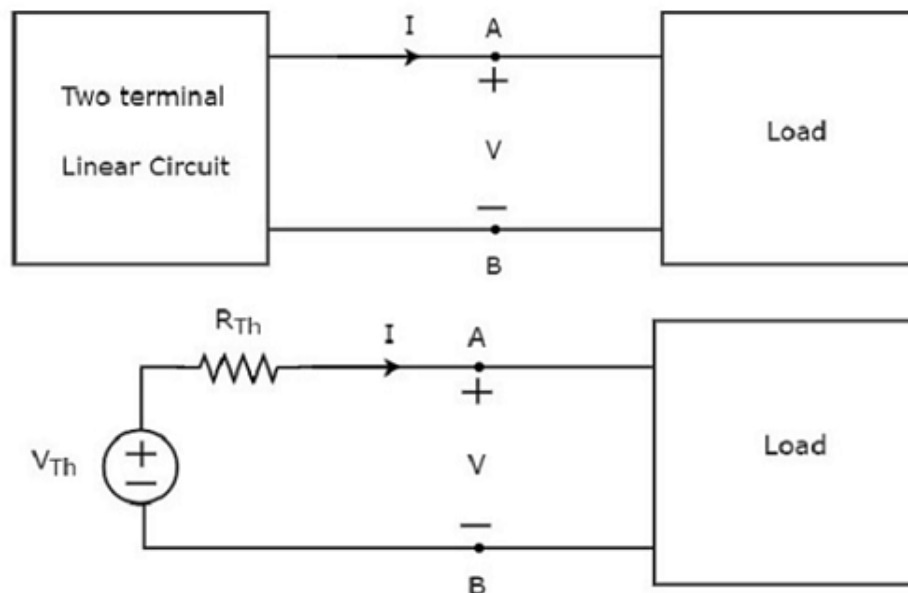Thevenin Theorem:- Thevenin's Theorem states that Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load




Norton Theorem:- Norton's Theorem states that Any linear circuit containing several energy sources and resistances can be replaced by a single Constant Current generator in

parallel with a Single Resistor.

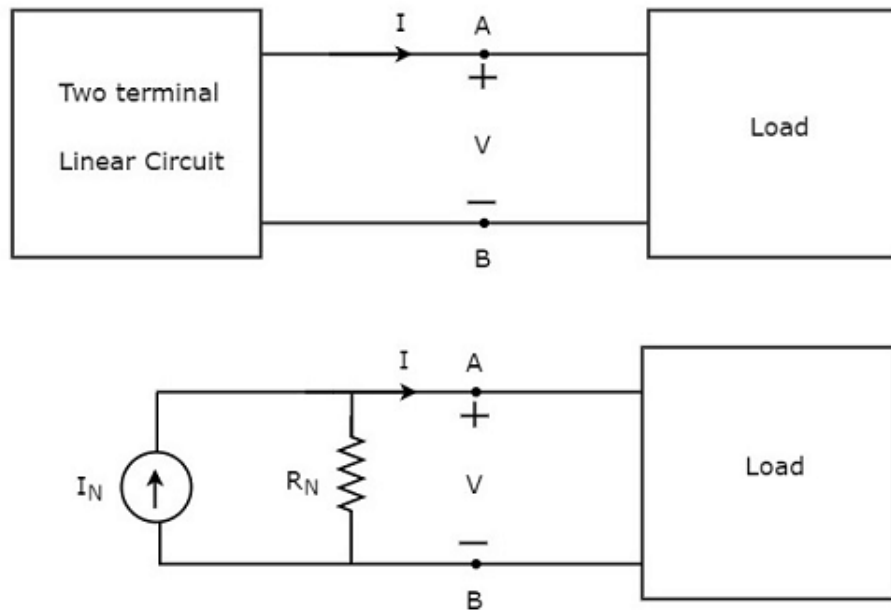

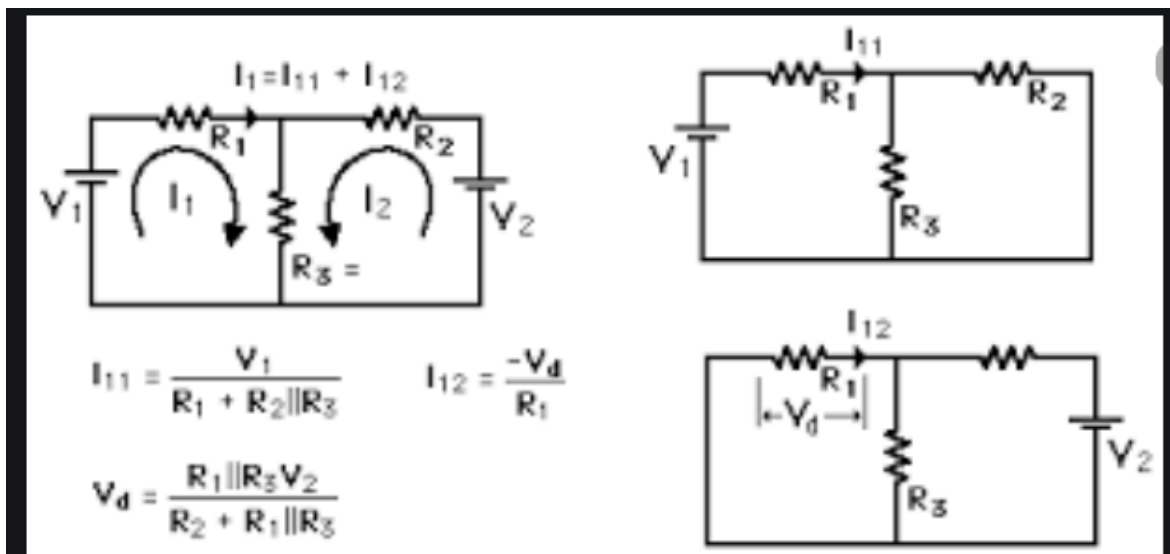Superposition Theorem:- Superposition theorem is based on the concept of linearity between the response and excitation of an electrical circuit. It states that the response in a particular branch of a linear circuit when multiple independent sources are acting at the same time is equivalent to the sum of the responses due to each independent source acting at a time.



3 Apparatus

DC power supply, multimeter, resistors (47Ω, 100 Ω, 1000Ω)

4 Theoretical Background

4.1 Thevenin Theorem

- Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent

circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} , where V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals

when the independent sources are turned off.

- As far as the load resistor R_L is concerned, any complex one-port network consisting of multiple resistive circuit elements and energy sources can be replaced by one single equivalent resistance R_s and one single equivalent voltage V_s . R_s is the source resistance value looking back into the circuit and V_s is the open circuit voltage at the terminals.
- It's applicable on both dependent and independent sources.
- It doesn't apply to non-linear circuit elements like transistors, diodes, etc.

4.2 Norton Theorem

- Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N , where I_N is the short-circuit

current through the terminals and R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.

- As far as the load resistance, R_L is concerned this single resistance, R_S is the value of the resistance looking back into the network with all the current sources open circuited and I_S is the short circuit current at the output terminals as shown below.
- It's applicable on both dependent and independent sources.
- It doesn't apply to non-linear circuit elements like transistors, diodes, etc.

4.3 Superposition Theorem

- Superposition theorem is based on the concept of linearity between the response and excitation of an electrical circuit. It states that the response in a particular branch of a linear circuit when multiple independent sources are acting at the same time is equivalent to the sum of the responses due to each independent source acting at a time.

- This theorem cannot be used to measure power and is not applicable to unbalanced bridge circuits.
- Applicable only to linear circuits.

5 Procedures

5.1 Thevenin Theorem

- Step 1 Consider the circuit diagram by opening the terminals with respect to which, the Thevenins equivalent circuit is to be found.
- Step 2 Find Thevenins voltage V_{Th} across the open terminals of the above circuit.
- Step 3-If dependent sources are not present the R_{Th} can be found switching off all the independent sources.
- Step 4 Find the short circuit current I_{SC} by shorting the two opened terminals of the above circuit.
- Step 5 Find Thevenins resistance R_{Th} by using the following formula.
- It's applicable of both dependent and independent sources.

$$R_{Th} = \frac{V_{Th}}{I_{SC}} \quad (1)$$

5.2 Norton Theorem

- Step 1 Consider the circuit diagram by opening the terminals with respect to which the Nortons equivalent circuit is to be found.
- Step 2 Find the open circuit voltage V_{OC} across the open terminals of the above circuit.
- Step 3 Find the Nortons current I_N by shorting the two opened terminals of the above circuit.
- Step 4-If dependent sources are not present the R_{Th} can be found switching off all the independent sources.
- Step 5 Find Nortons resistance R_N by using the following formula.


- It's applicable of both dependent and independent sources.

$$R_N = \frac{V_{OC}}{I_N} \quad (2)$$

5.3 Superposition Theorem

- Step 1 Find the response in a particular branch by considering one independent source and eliminating the remaining independent sources present in the network.
- Step 2 Repeat Step 1 for all independent sources present in the network.
- Step 3 Add all the responses in order to get the overall response in a particular branch when all independent sources are present in the network.

5.4 Task -1

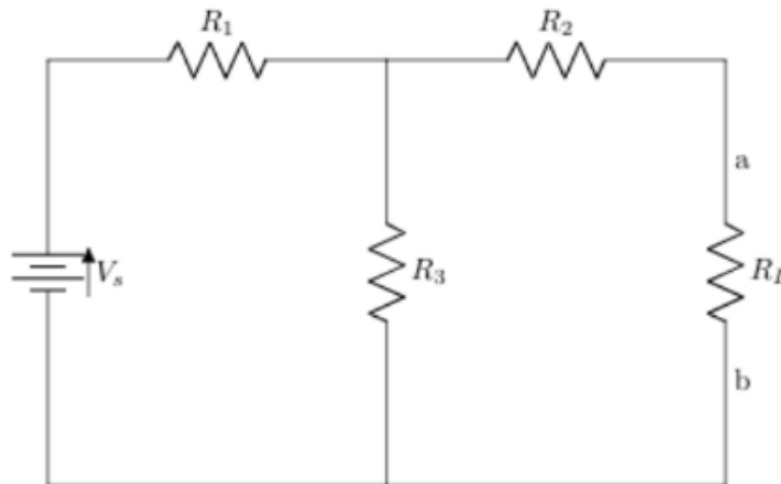

The R_1, R_2, R_3 are respectively,

Considering V_s as 11.5V

We will use the current division and voltage division rules to explicitly find the following results.

The first step is to find the effective resistance since no dependent source is present hence we can directly

Shorting V_s we get $R_1 // R_3 + R_2$

$$R_{eff} = \frac{R_1 \times R_3}{R_1 + R_3} + R_2 \quad (3)$$

Next the voltage V_{Th}

could be found by open circuiting terminals a and b.

Hence voltage across R_3 would be same as the load R_L .

$$V_{Th} = \frac{V_S}{\frac{R_3 \times R_1}{R_1 + R_3}} \times R_3 \quad (4)$$

Next step is to find the I_N ,

it can be done by short circuiting a and b terminals, the current through the terminals is same as the current

$$I_N = \frac{V_S}{R_1 + \frac{R_2 \times R_3}{R_2 + R_3}} \times \frac{R_3}{R_2 + R_3} \quad (5)$$

Therefore the voltage drop across the load is when V_{Th} and R_{eff} are in series with the R_L .

$$V_L = \frac{V_s}{\frac{R_1 \times R_3}{R_1 + R_3} + R_2 + R_L} \times R_L \quad (6)$$

And the current is given by


$$I_L = V_{Th} / R_L + R_{eff} \quad (7)$$

The current through Norton's method :

$$I_L = \frac{R_{eff}}{R_L + R_{eff}} \times I_N \quad (8)$$

We conclude that $I_N \times R_{eff} = V_{Th}$.

5.5 Task -2

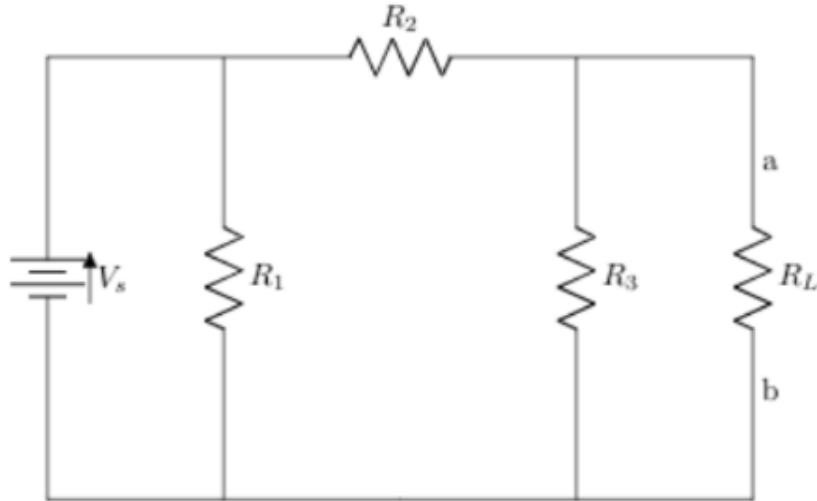

The R_1, R_2, R_3 1000 Ω , 47 Ω , 100 Ω are respectively,

Considering V_s as 11.5V

We will use the current division and voltage division rules to explicitly find the following results.

The first step is to find the effective resistance since no dependent source is present hence we can directly

Shorting V_s we get $R_2 // R_3$

$$R_{eff} = \frac{R_2 \times R_3}{R_3 + R_2} \quad (9)$$

Next the voltage V_{Th}

could be found by open circuiting terminals a and b .

Hence voltage across R_3 would be same as the load R_L .

$$V_{Th} = \frac{V_s}{\frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3}} \quad (10)$$

Next step is to find the I_N ,

it can be done by short circuiting a and b terminals, the current through the terminals is same as the current I_N .

$$I_N = \frac{V_s}{\frac{R_2 \times R_1}{R_2 + R_1}} \times \frac{R_1}{R_2 + R_1} \quad (11)$$

Therefore the voltage drop across the load is when V_{Th} and R_{eff} are in series with the R_L .

$$V_L = \frac{V_{Th}}{\frac{R_2 \times R_3}{R_3 + R_2} + R_L} \quad (12)$$

And the current is given by

$$I_L = V_{Th} / R_L + R_{eff} \quad (13)$$

The current through Norton's method :


$$I_L = \frac{R_{eff}}{R_L + R_{eff}} \times I_N \quad (14)$$

We conclude that $I_N \times R_{eff} = V_{Th}$.

5.6 Task 3

The values of R_1, R_2, R_3 are $100\Omega, 100\Omega, 1000\Omega$ respectively.

And V_1 and V_2 are $5V$ each.

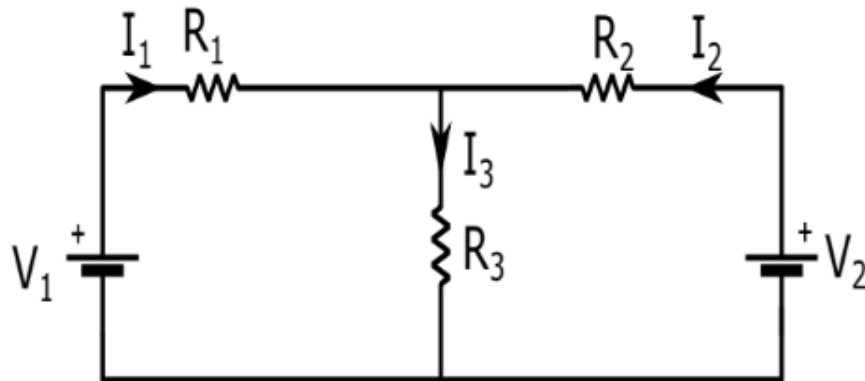

When source-1 is excited

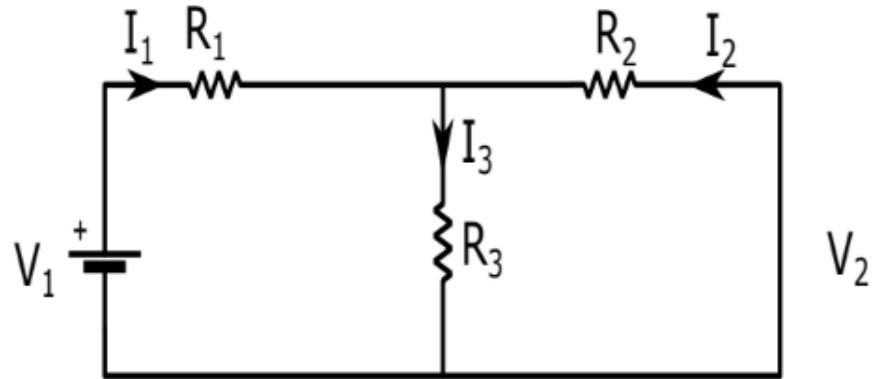


Figure 10: With source-1

$$I'_1 = V_1 \frac{R_2 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I'_2 = V_1 \frac{R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I'_3 = V_1 \frac{R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

When source-2 is excited

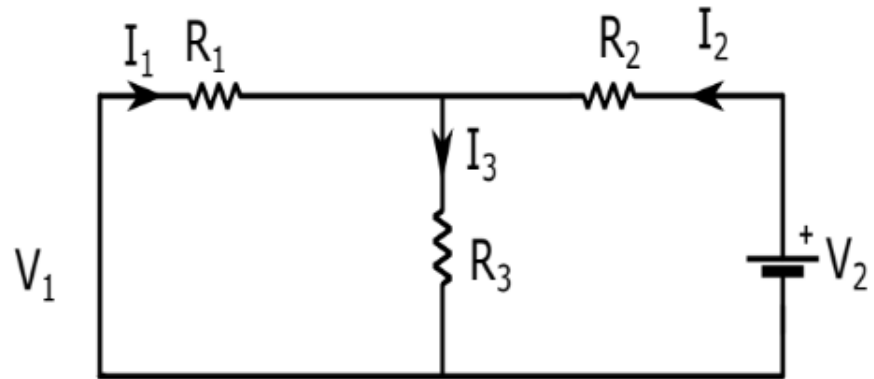


Figure 11: with source-2

$$I_2'' = V_2 \frac{R_1 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I_1'' = V_1 \frac{R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$I_3'' = V_1 \frac{R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

Total Response is the combination of above two responses.

$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$

$$I_3 = I_3' + I_3''$$

6 Analysis

6.1 Task-1

Table 1: Thevenin's and Norton's results

Parameters	Theoretical values	Experimental values
1. $R_{Th} \text{ or } R_N$	147 Ω	146.6 Ω
2. V_{Th}	11 V	10.97V
3. I_N	74.5mA	73.9mA
4. V_L	4.5V	4.48V
5. I_L	44mA	43.8mA

6.2 Task-2

Table 1: Norton's and Thevenin's results

Parameters	Theoretical values	Experimental values
1. $R_{Th} \text{ or } R_N$	33.5 Ω	33.2 Ω
2. V_{Th}	7.66V	7.77V
3. I_N	0.246A	0.24A
4. V_L	5.86V	5.83V
5. I_L	56.9mA	57.6mA

6.3 Task-3

Table 2: Superposition results

Parameters	Theoretical values	Experimental values
1. V_3	4.75V	4.76V
2. V_2	0.25V	0.26V
3. V_{13}	2.375V	2.36V
4. V_{23}	2.375V	2.38V
5. V_{12}	-2.35V	-2.36V
6. V_{22}	2.6v	2.63V
7. I_3	4.6mA	4.59mA
8. I_2	2.45mA	2.45mA
9. I_{13}	2.3mA	2.38mA
10. I_{23}	2.3mA	2.37mA
11. I_{12}	-23.45mA	23.3mA
12. I_{22}	25mA	25.7mA

7 Conclusions

We verified the Thevenin ,Norton and Superposition theorem.
By connecting the resistors according to the circuit ,we found the currents and voltages through load resistor theoretically and experimentally.

) Reasons for variation in the values:

- Due to heating effect.
- Even it may be because of negligence of resistance of multimeter.
- Because of variations of voltages from DC power supply.

In Thevenin and Norton thorems, power dissipation may not be same as the theoritical values and valid only for a linear range.

Source Modelling and resistance measuring are some of the pratical applications.
Superposition theorem is not used for power calculations and not valid for time-varying resistances.