

Voltage and current division as an application of KVL and KCL.

Report 2

P.Srijith Reddy,
EE19BTECH11041,
J.Eshwari
EE19BTECH11042

Department of Electrical Engineering
IIT Hyderabad

February 25, 2020

Abstract

In this experiment we studied the behaviour of voltage division and current division rule as an application of KCL and KVL in reality which turns out to be close to ideal behaviour using ammeter and voltmeter.

1 Introduction

The very important physical effect has applications to chip manufacturing ,electric appliances ,almost every aspect of modern world.

2 Theoretical Background

Voltage division is used to calculate the voltage drop across a resistor (impedance) as a fraction of total voltage across a series string of resistors (impedances).

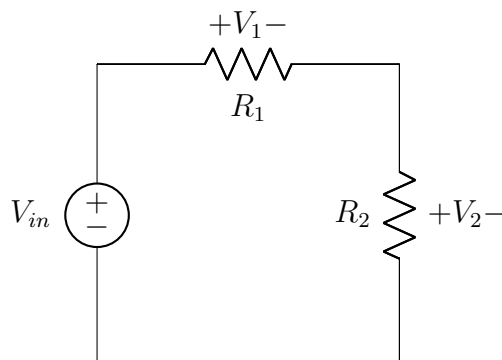



Figure 1: Voltage Divider

Current Division is used to calculate the fraction of the total current into a parallel string of resistors flows through any one of the resistors.

$$V_1 = V_{in} \frac{R_1}{R_1 + R_2} \quad (1)$$

$$V_2 = V_{in} \frac{R_2}{R_1 + R_2} \quad (2)$$

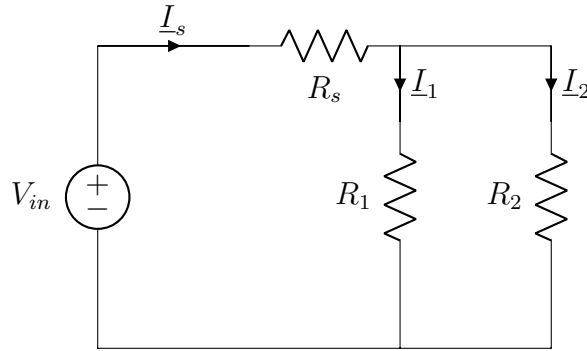Current Division is used to calculate the fraction of the total current into a parallel string of resistors flows through any one of the resistors.



$$I_1 = I_s \frac{R_2}{R_1 + R_2} \quad (3)$$

$$I_2 = I_s \frac{R_1}{R_1 + R_2} \quad (4)$$

3 Procedures

Connect the circuit as shown in Fig. 3 and determine the value of \$I_1\$ and \$I_2\$. In Fig. 3, add one more resistor in parallel with \$R_1\$ and \$R_2\$ and check the variation in \$I_1\$, \$I_2\$ and \$I_s\$.

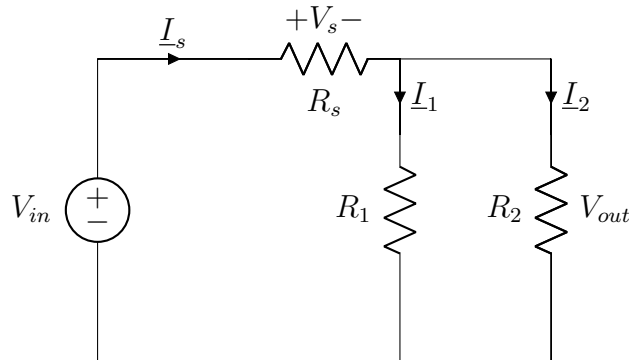


Figure 3: Circuit 1

Now we verify volatage division rule and current division rule using the practical values obtained by placing ammeter and voltmeter .

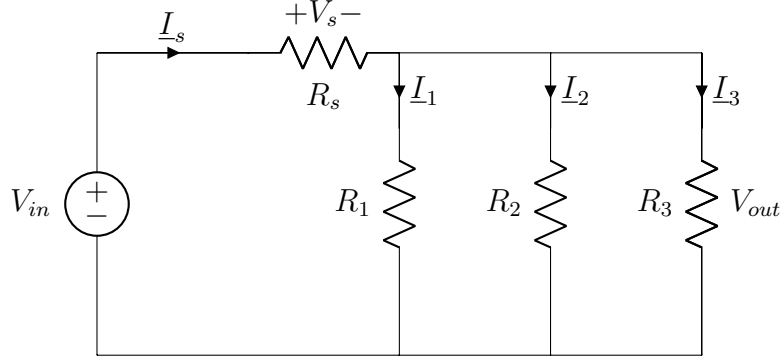


Figure 4: After adding resistor to the circuit 1

Now we should repeat the experiment for circuit below and also make sure that the power in resistor does not exceed it's limit.

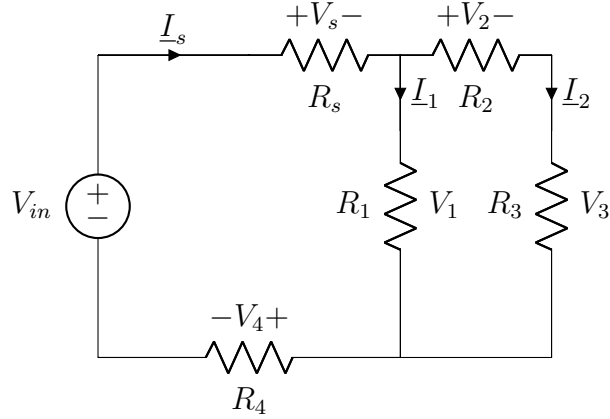


Figure 4 :Circuit 2

4 Analysis

Experiment 1 components

$$V_{in} = 24.7V$$

$$R_s = 47\Omega$$

$$R_1 = 220\Omega$$

$$R_2 = 1K\Omega$$

Theoretical values Using KCL

$$I_s = I_1 + I_2 \quad (5)$$

Using KVL

$$V_{in} = I_s R_s + I_1 R_1 \quad (6)$$

$$I_1 R_1 = I_2 R_2 \quad (7)$$

We find the values of I_s, I_1, I_2 using the above equations.

Element	Theoretical value	Experimental value
I_s	108.6 mA	106 mA
I_1	89.06 mA	87 mA
I_2	19.59 mA	19.56 mA
V_s	5.10 V	5.13 V
V_{out}	19.59 V	19.52 V

After adding resistor in parallel to circuit 1

$R_3 = 1K\Omega$

Theoretical values

Using KCL

$$I_s = I_1 + I_2 + I_3 \quad (8)$$

Using KVL

$$V_{in} = I_s R + I_1 R_1 \quad (9)$$

$$I_1 R_1 = I_2 R_2 = I_3 R_3 \quad (10)$$

Element	Theoretical value	Experimental value
I_s	123 mA	121 mA
I_1	85.86 mA	83 mA
I_2	18.88 mA	19 mA
I_3	18.88 mA	19 mA
V_s	5.81 V	5.86 V
V_{out}	18.88 V	18.85 V

Experiment 2

components

$V_{in} = 24.7V$

$R_s = 47\Omega$

$R_1 = 220\Omega$

$R_2 = 1K\Omega$

$R_3 = 1K\Omega$

$R_4 = 47\Omega$

Theoretical values

Using KCL

$$I_s = I_1 + I_2 \quad (11)$$

$$V_{in} = I_s R_s + I_1 R_1 + I_s R_4 \quad (12)$$

$$I_1 R_1 = I_2 (R_2 + R_3) \quad (13)$$

Element	Theoretical value	Experimental value
I_s	84.5 mA	83.5 mA
I_1	76.15 mA	75 mA
I_2	8.37 mA	8.4 mA
V_s	3.97 V	3.97 V
V_1	16.75 V	16.7 V
V_2	8.37 V	8.35 V
V_3	8.37 V	8.35 V
V_4	3.97 V	3.98 V

5 Conclusions

- The table shows that theoretical values and experimental values are close and so we have felt the power of voltage and current division rule in reality.
- We should also note that KCL and KVL doesn't hold good all the time .
- KCL doesn't hold good when there is a leakage of charge or accumulation of charge at node.
- KVL is also invalid when the electric field within a loop is not conservative. Based on the laws of physics (Maxwells equations), this occurs in the presence of a changing magnetic field within the circuit, which can certainly arise within high-frequency AC circuits

Thank you